

大葉大學 九十四 學年度 研究所碩士班 招生考試試題紙

系 所 別	組 別	考 試 科 目 ( 中 文 名 稱 )	考 試 日 期	節 次	備 註
電機工程學系碩士班 電信工程學系碩士班	甲、乙組	電子學	3月27日	第二節 10:30~12:00	

註：考生可否攜帶計算機或其他資料作答，請在備註欄註明（如未註明，一律不准攜帶）

\* 計算題答案應詳列計算步驟，否則一概不予計分。

\* 可使用計算機。

\* 本試題共二頁。

P2-1

一、單選選擇題：

(27%，每題3%，答錯倒扣1%，未答不扣分，答案卷上須按題目順序答題，否則不予計分)

- By increasing the reverse bias voltage of a pn junction diode (before breakdown), the junction capacitance will (A) decrease (B) increase (C) increase first, then decrease (D) decrease first, then increase.
- Which one of the following is true for an ideal op amp? (A)  $R_{in} = 0$  and  $R_{out} = 0$  (B)  $R_{in} = \infty$  and  $R_{out} = 0$  (C)  $R_{in} = 0$  and  $R_{out} = \infty$  (D)  $R_{in} = \infty$  and  $R_{out} = \infty$ .
- In the following feedback topologies, which one can increase the input resistance and increase the output resistance? (A) shunt-series (B) series-shunt (C) shunt-shunt (D) series-series.
- Which one of the following is NOT an advantage of negative feedback? (A) Extend the bandwidth, (B) Reduce nonlinear distortion, (C) Desensitize the gain, (D) Increase the gain.
- Which one of the following statements is NOT true? (A) The common-emitter configuration suffers from the Miller effect. (B) The cascode configuration consists of a common-source transistor followed by a common-base transistor. (C) The Class A power amplifier suffers from crossover distortion. (D) For the feedback amplifier to be stable, its pole must all be in the left half of the s plane.
- The highest power conversion efficiency of a Class B power amplifier is (A) 0% (B) 25% (C) 50% (D) 78.5%.
- Which one is the fastest logic circuit family? (A) NMOS (B) PMOS (C) TTL (D) ECL.
- For a BJT operated at room temperature, the collector current is 1mA. Its  $g_m$  is: (A) 25m/Ω (B) 40m/Ω (C) 25 mV (D) 40Ω.
- Which one of the following statements is NOT true? (A) Zener diodes operate in the breakdown region. (B) The Early effect will result in a decrease in the effective base width. (C) Early effect will result in decrease in the collector current. (D) The emitter follower is useful as a voltage buffer.

二、計算題：(73%)

- An alternative bridge amplifier configuration with high input resistance is shown in Fig-1.
  - (5%) What is the gain  $V_o/V_i$ ?
  - (5%) For op amps using  $\pm 15V$  supplies that limit at  $\pm 13V$ , what is the largest sine wave you can provide across  $R_L$ ?
  - (5%) Using 2 kΩ as the smallest resistor, find resistor values that make  $V_o/V_i = 10 V/V$ .
- The MOSFETs in the circuit of Fig-2 are matched, with  $k_n'(W/L)_1 = k_p'(W/L)_2 = 100 \mu A/V^2$  and  $|V_t| = 2V$ . The resistance  $R = 10M\Omega$ .
  - (5%) For G and D open, what are the drain currents  $I_{D1}$  and  $I_{D2}$ ?
  - (5%) For finite  $r_o$  ( $r_o = |V_A| / I_D$ ,  $|V_A| = 200V$ ), what is the voltage gain from G to D and the input resistance at G?
  - (5%) If G is driven through a large coupling capacitor from a source  $V_i$  having a resistance of 1MΩ, find the voltage gain  $V_o/V_i$ .
  - (5%) For what range of output signals do Q1 and Q2 remain in the pinch-off region?

大葉大學 九十四 學年度 研究所碩士班 招生考試試題紙

系 所 別	組 別	考 試 科 目 (中文名稱)	考 試 日期	節 次	備 註
電機工程學系碩士班 電信工程學系碩士班	甲、乙組	電子學	3月27日	第二節 10:30~12:00	

註：考生可否攜帶計算機或其他資料作答，請在備註欄註明（如未註明，一律不准攜帶）

P2-2

- (12%) For the circuit shown in Fig-3, utilize the constant-voltage drop model (0.7V) for each conducting diode and sketch the transfer characteristics  $V_o-V_i$  of the circuit.
- (6%) A BJT for which  $\beta_F = 100$  and  $\alpha_R = 0.2$  operates with a constant base current but with the collector open. What value of  $V_{CEsat}$  would you measure?
- Sketch the Bode magnitude and phase plots for the following functions:

(a)  $T(s) = \frac{100s}{(s+100)(s+100000)}$  (10%)

(b)  $T(s) = \frac{10^5(10^5 + s)}{(10^3 + s)(10^4 + s)}$  (10%)

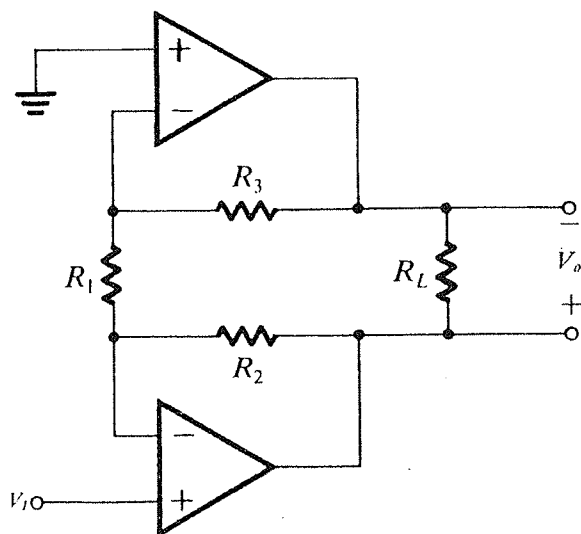


Fig-1

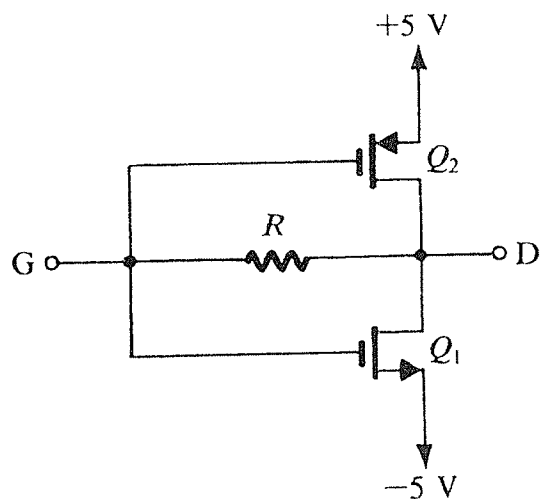


Fig-2

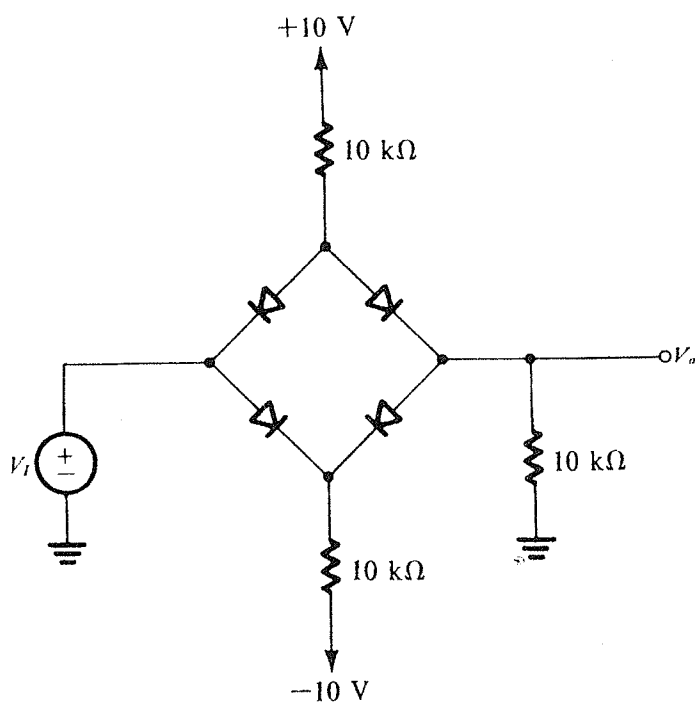


Fig-3